

Logic gate	Symbol	Truth table																		
XOR An XOR gate's output is 1 only when both its inputs are different. This is sometimes known as Exclusive-OR.		<table> <tr> <th colspan="2">INPUT</th><th>OUTPUT</th></tr> <tr> <th>A</th><th>B</th><th>A XOR B</th></tr> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </table>	INPUT		OUTPUT	A	B	A XOR B	0	0	0	0	1	1	1	0	1	1	1	0
INPUT		OUTPUT																		
A	B	A XOR B																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	0																		
XNOR An XNOR gate is equivalent to an XOR gate followed by a NOT gate. Its output is 1 only when both its inputs are the same.		<table> <tr> <th colspan="2">INPUT</th><th>OUTPUT</th></tr> <tr> <th>A</th><th>B</th><th>A XNOR B</th></tr> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>1</td></tr> </table>	INPUT		OUTPUT	A	B	A XNOR B	0	0	1	0	1	0	1	0	0	1	1	1
INPUT		OUTPUT																		
A	B	A XNOR B																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	1																		
NAND A NAND gate is equivalent to an AND gate followed by a NOT gate. Its output is 1 unless both its inputs are 1.		<table> <tr> <th colspan="2">INPUT</th><th>OUTPUT</th></tr> <tr> <th>A</th><th>B</th><th>A NAND B</th></tr> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </table>	INPUT		OUTPUT	A	B	A NAND B	0	0	1	0	1	1	1	0	1	1	1	0
INPUT		OUTPUT																		
A	B	A NAND B																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
NOR A NOR gate is equivalent to an OR gate followed by a NOT gate. Its output is 1 only when both its inputs are 0.		<table> <tr> <th colspan="2">INPUT</th><th>OUTPUT</th></tr> <tr> <th>A</th><th>B</th><th>A NOR B</th></tr> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </table>	INPUT		OUTPUT	A	B	A NOR B	0	0	1	0	1	0	1	0	0	1	1	0
INPUT		OUTPUT																		
A	B	A NOR B																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		

Combining gates

Computers carry out addition using circuits called binary adders. As computers do everything in 0s and 1s, binary adders must be combined to add numbers of several digits. They do this by having two outputs, sum and carry. The sum is the result of adding the inputs together. If both are 1, the output should be 2, which in binary is 10. The carry output becomes 1 to move the digit representing 2 into the next adder along.

▷ Half-adders

Each adder contains two smaller circuits called half-adders made of only two logic gates, an XOR and an AND.

