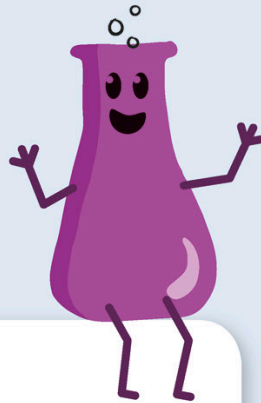


Electricity

Electricity is a type of **energy**. It powers many machines and devices, from fast trains to smart phones. For electricity to work, the things it powers must be connected by a circuit.

Circuit

A circuit is a complete loop around which electricity can **flow**. The flow of electricity is called a **current**. If there is a gap in the loop, current cannot flow. A circuit must include a source of electricity, such as a **battery**.



Bulb

This bulb glows with light when electricity flows through it. The bulb will only light up if it is part of an electric circuit.

A circuit may include parts such as a switch, bulb, buzzer, or motor. These parts are called **components**.

Battery basics

A battery has two ends called **terminals**—one is negative (-) and the other is positive (+). When wires are connected to the terminals, electricity flows out of the battery, zooms around the circuit, and then returns to the battery.



Battery

Inside a battery are **chemicals** that make electricity. Wires must be connected to each end of the battery for current to flow.

