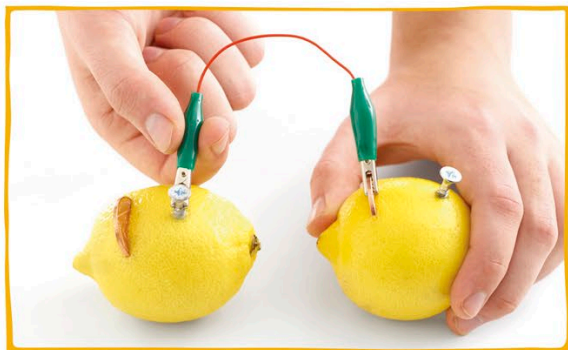





3 Squeeze the clip on one wire so that it opens, like a crocodile's jaws. Place it around the screw in one lemon, so it grips it. Connect the other clip to the coin in another lemon.




5 Each LED has two legs, which are slightly different lengths. With the free end of the wire that is attached to the coin, fix the clip to the slightly longer leg of the LED.

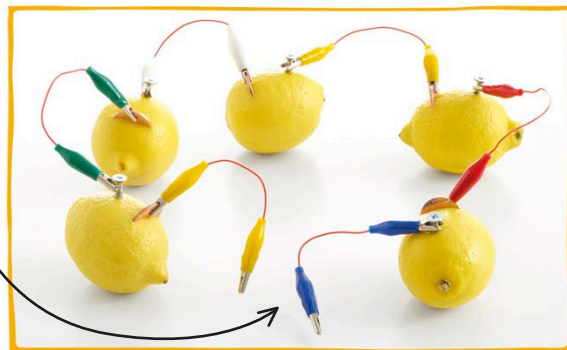The wires from the first and last lemons both have one end unconnected.



4 Connect all the lemons—coin to screw—as in step 3. For the last lemon, attach a wire to its coin, but don't connect it to the screw in your first lemon. Instead, attach another wire to that screw.

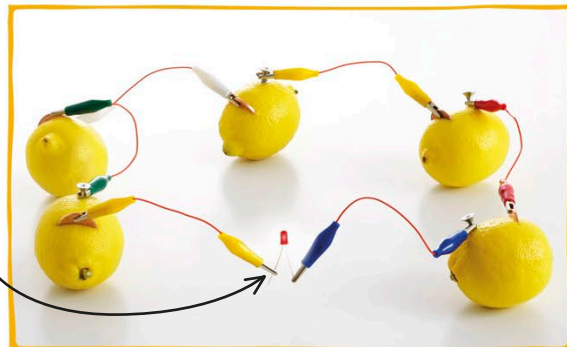If the light from the LED is weak, try pushing in or wiggling the screws and coins.



6 Now connect the clip of the other free wire that is connected to the screw to the other, shorter leg of the LED. This now completes the circuit to make the LED light up.

HOW IT WORKS

The electric current that lights your LED is actually caused by countless tiny particles called electrons moving around the circuit. Electrons are present inside every atom. As the zinc dissolves in the lemon juice, two electrons are released from each atom of zinc (from the screw). All electrons are negatively charged, and they push apart as they move inside the wire. When they reach the copper coin, they take part in another chemical reaction, allowing electrons to continue flowing around the circuit.

